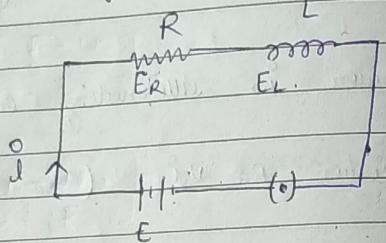


STEADY & VARYING CURRENT

growth and decay of current through R-L circuit.



Potential drop at Resistance
 $E_R = iR$

Potential drop at inductor by Faradays law.

$$E_L = \bullet L \frac{di}{dt}$$

$$\boxed{E_L = \bullet L \frac{di}{dt}}$$

Total potential drop in circuit

= $\sqrt{\text{Potential drop in } R \text{ & } L}$.

Sum of

$$E = E_R + E_L$$

$$E = iR + L \frac{di}{dt}$$

$$E = iR + L \frac{di}{dt}$$

$$E - iR = L \frac{di}{dt}$$

$$\frac{(E - iR)}{L} = \frac{di}{dt}$$

$$\frac{dt}{L} = \frac{di}{E - iR}$$

$$\text{let } E - iR = t$$

$$-R di = dt$$

$$\boxed{\frac{di}{dt} = -\frac{dt}{R}}$$

$\int \frac{dt}{L}$ \Rightarrow Integrate both sides

$$\int \frac{dt}{L} = \int \frac{-dt}{R \cdot t} = -\frac{1}{R} \log t + C$$

$$\frac{t}{L} = -\frac{1}{R} \log(E - iR) + C \quad \text{--- (i)}$$

at $t=0$ current $i=0$

$$C = \frac{1}{R} \log(E)$$

$$\boxed{C = \frac{1}{R} \log E} \quad \text{--- (ii)}$$

Put (ii) in (i)



$$\frac{1}{e} = 0.368$$

$$\frac{t}{L} = \frac{\log(E - iR)}{-R} + \frac{1}{R} \log E$$

$$\frac{t}{L} = \frac{1}{R} \log \left(\frac{E}{E - iR} \right)$$

$$\frac{t}{L} = \frac{1}{R} \log \left[\frac{E - iR}{E} \right]$$

$$\frac{-Rt}{L} = \log \left[1 - \frac{iR}{E} \right]$$

$$1 - \frac{iR}{E} = e^{-\frac{Rt}{L}}$$

$$\frac{iR}{E} = 1 - e^{-\frac{Rt}{L}}$$

$$i = \frac{E}{R} \left[1 - e^{-\frac{Rt}{L}} \right]$$

initial current

$$\frac{E}{R} = \text{maximum current} = i_0$$

$$i = i_0 \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$\frac{L}{R} = \gamma \text{ time constant}$$


$$\boxed{\frac{L}{R} = \frac{t}{-}}$$

$$i = i_0 \left[1 - e^{-\frac{Rt}{L}} \right]$$

$$i = i_0 \left[1 - \frac{1}{e} \right] = i_0 \left[1 - \frac{1}{2.718} \right]$$

$$i = i_0 (0.632)$$

$$\boxed{i = 0.632 i_0}$$

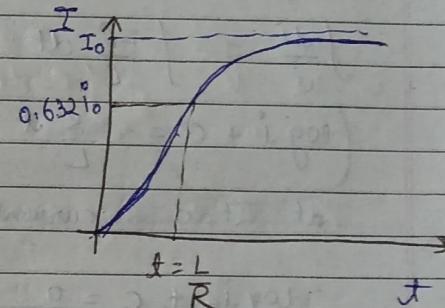

Decay of current :

when the key is pressed for $t > \frac{L}{R}$, current attains its maximum value i_0 . On releasing key, current in the circuit is decreases from i_0 to 0. in this case external e.m.f. $E=0$.

let i be the value of current at any instant of time ' t'

$$E = V_L + V_R$$

$$E_R = -E_L$$

$$iR = -L \frac{di}{dt}$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

integrate both sides.

$$\int \frac{di}{i} = \int -\frac{R}{L} dt$$

$$(\log i + C = -\frac{R}{L} t) \quad \text{--- (i)}$$

at $t=0$ current $i = i_0$ (max).

$$\log i_0 + C = 0$$

$$C = -\log i_0$$


put value of integration constant in eq(i)

$$\log i - \log i_0 = -\frac{Rt}{L}$$

$$\log \frac{i}{i_0} = -\frac{Rt}{L}$$

$$\frac{i}{i_0} = e^{-\frac{Rt}{L}}$$

$$i = i_0 e^{-\frac{Rt}{L}}$$

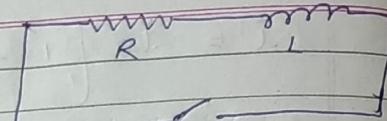


$$I = I_0 e^{-\frac{R}{L}t}$$

Here $\frac{L}{R}$ is called inductance time constant

$$\text{when } \frac{L}{R} = t$$


$$I = I_0 e^{-\frac{t}{\frac{L}{R}}} = \frac{I_0}{e^t}$$

$$I = 0.368 I_0$$

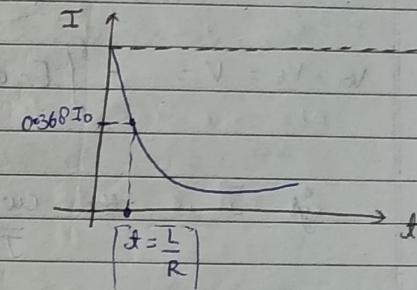

Resistance of a cylindrical conductor and specific resistance.

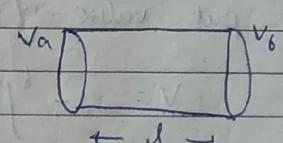Consider a cylinder of length l let V_a and V_b be the potential diff across the ends of the conductor.



We know that

$$R = \frac{V}{I}$$

$$\text{Resistance is given by } R = \frac{V_b - V_a}{I}$$

$$R_{AB} = \frac{V_B - V_A}{I}$$

also we know the relation between potential diff and electric field

$$\nabla V = -E \hat{d}r$$

$$\text{so } V_A - V_B = - \int_a^b E \cdot dr \quad (\text{for cylinder})$$

$$V_A - V_B = V = - \int_a^b E \cdot dr \quad (i)$$

if \vec{J} is the current density then
 $\vec{J} = \sigma \vec{E}$

where $\sigma \rightarrow$ electrical conductivity

$$E = \frac{\vec{J}}{\sigma} = \frac{i}{A\sigma} \quad \therefore \vec{J} = \frac{i}{A}$$

$$\vec{E} = \frac{i}{A\sigma}$$

put value of \vec{E} in eq (i)

$$V = - \int_a^b \frac{i}{A\sigma} \cdot dr$$

$$\therefore \int_a^b f(m) = - \int_a^b f(n)$$

$$V = \int_a^b \frac{i}{\pi r^2 \sigma} \cdot dr$$

$$V = \frac{i}{\pi r^2 \sigma} \int dr = \frac{i l}{\pi r^2 \sigma}$$

$$\frac{V}{l} = \frac{i}{\pi r^2 \sigma}$$

$$\text{we know } \frac{V}{l} = R = \frac{i}{A\sigma} \Rightarrow \frac{1}{\sigma} = \frac{RA}{l}$$

$$\frac{1}{\sigma} = \text{resistivity} = \rho = \frac{RA}{l}$$

$$\rho = \frac{RA}{l}$$

$$R = \frac{\rho l}{A}$$

Weidmann's Frenz law

The ratio of Thermal conductivity (K) to the electrical conductivity is directly proportional to the temperature.

$$\frac{K}{\sigma} \propto T$$

$$\frac{K}{\sigma} \propto T$$

$$\frac{K}{\sigma} = LT$$

Lorentz number




II Equation of continuity

As we know that the electrical charge is indestructible, it is never lost or created. That is the charge is conserved.

we know current density (\vec{J})

$$\vec{J} = \frac{\vec{i}}{A}$$

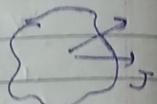

$$\text{so } \vec{i} = \vec{J} \cdot A$$

$$\text{also we can write } \vec{i} = \int_S \vec{J} \cdot d\vec{s} \quad (i)$$

$$\text{current } \vec{i} = -\frac{dQ}{dt}$$

$$Q = \frac{C}{V}$$

and charge (Q):

$$\text{atm electrical charge density } (\rho) = \frac{Q}{V}$$

$$Q = \rho V$$

$$Q = \int_V \rho dV \quad (ii)$$

$$\text{so } \vec{i} = -\frac{d}{dt} \int_V \rho dV \quad (iii)$$

Compare (iii) with (i)

$$\int_S \vec{J} \cdot d\vec{s} = -\frac{d}{dt} \int_V \rho dV$$

$$\int_S \vec{J} \cdot d\vec{s} = -\int \frac{\partial}{\partial t} \rho dV \quad (iv)$$

using gauss divergence theorem.

$$\int_S \vec{J} \cdot d\vec{s} = \int_V \vec{\nabla} \cdot \vec{J} dV$$

so eq (iv) can be written as.

$$\int_V \vec{\nabla} \cdot \vec{J} dV = -\int \frac{\partial}{\partial t} \rho dV$$

$$\int_V \left(\vec{\nabla} \cdot \vec{J} + \frac{\partial}{\partial t} \rho \right) dV = 0$$

$$\vec{\nabla} \cdot \vec{J} + \frac{\partial}{\partial t} \rho = 0$$

$$\boxed{\vec{\nabla} \cdot \vec{J} = -\frac{\partial \rho}{\partial t}} \rightarrow \text{eq equation of continuity}$$

$$\boxed{\vec{\nabla} \cdot \vec{J} = -\frac{\partial \rho}{\partial t}}$$

Steady This is an imp equation regarding "charge flow called continuity equation" and the fact the charge is conserved.

In a steady state in which all time derivatives are 0 so we must have

$$\frac{\partial \rho}{\partial t} = 0 \text{ and } \nabla \cdot \vec{J} = 0.$$

$$\int J \cdot ds = 0$$

$$\nabla \cdot \vec{J} = \nabla \cdot \sigma \vec{E} = \sigma \nabla \cdot \vec{E} = 0.$$

So for a steady state we conclude the E has 0 divergence.

$$\vec{E} = -\nabla V \quad \text{Potential}$$

$$-\nabla \cdot \nabla V = \sigma \nabla^2 V = 0$$

$$\boxed{\nabla^2 V = 0} \rightarrow \text{Laplace equation}$$

Relaxation time

equation of continuity

$$\operatorname{div} \vec{J} + \frac{\partial \rho}{\partial t} = 0$$

$$\vec{J} \cdot \vec{J} + \frac{\partial \rho}{\partial t} = 0.$$

where $\vec{J} \rightarrow$ current density

$\rho \rightarrow$ charge density

vector form of ohm's law

$$\vec{J} = \sigma \vec{E}$$

$$\vec{J} \cdot (\sigma \vec{E}) + \frac{\partial \rho}{\partial t} = 0$$

$$\sigma (\vec{J} \cdot \vec{E}) + \frac{\partial \rho}{\partial t} = 0$$

Conductivity of conductor

$$\operatorname{div} \vec{E} = \frac{\rho}{\epsilon_0}$$

→ differential form of ohm's law

$$\sigma (\vec{J} \cdot \vec{E}) + \frac{\partial \rho}{\partial t} = 0$$

$$\sigma \frac{\rho}{\epsilon_0} + \frac{\partial \rho}{\partial t} = 0$$


$$\frac{\partial \rho}{\partial t} = -\sigma \frac{\rho}{\epsilon_0}$$

$$\frac{\partial \rho}{\partial t} = -\frac{\sigma}{\epsilon_0} \rho \delta t$$

integrate both sides

$$\int \frac{\partial \rho}{\rho} = \int -\frac{\sigma}{\epsilon_0} \delta t$$

$$\log |\rho| = -\frac{\sigma}{\epsilon_0} t + A$$

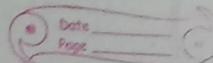

$$\log \beta = -\frac{ct}{\epsilon_0} + A$$

at time $t=0$ $\beta = \beta_0$

$$\log \beta_0 = A$$

$$\log \beta = -\frac{ct}{\epsilon_0} + \log \beta_0$$

$$\log \frac{\beta}{\beta_0} = -\frac{ct}{\epsilon_0}$$

$$\frac{\beta}{\beta_0} = e^{-\frac{ct}{\epsilon_0}}$$

$$\beta = \beta_0 e^{-\frac{ct}{\gamma}}$$

where γ = relaxation time = $\frac{\epsilon_0}{c}$.

Kirchoff's law

(i) Kirchoff's first law / current law.

It applies to the circuit nodes (or junction) and states that in any network or junction the algebraic sum of the currents at any junction in a circuit is zero.

$$\sum I = 0$$

Kirchoff's Voltage law or loop Rule

- * It applies to close circuit (meshes) and states that in any closed circuit, algebraic sum of the products of the current & resistance of the each part of the circuit is equals to the total emf acting in circuit

$$\sum i R = \sum E$$

Lorentz - drude theory

v_d , γ , I & v_d , J , Deduction to Ohm's law.

- * If $v_1, v_2, v_3, \dots, v_n$ are random velocity of e- in an conductor.

$$\text{average velocity} = v = \frac{v_1 + v_2 + \dots + v_n}{n}$$

No net flow of charge in any direction because with same speed e- moves in opposite direction

On applying \vec{E} , then the force applied on electron

$$f = -e\vec{E}$$



$$\text{Acceleration} = a = \frac{f}{m} = \frac{f_{\text{ext}}}{m} = -\frac{eE}{m}$$

$$a = -\frac{eE}{m}$$

\vec{v}_2

g. an e⁻ having random thermal velocity \vec{v}_1 and accelerate for time γ_1 .

$$\text{then } [\vec{v}_1 = \vec{v}_1 + a \vec{\gamma}_1]$$

$$\text{Similarly, } [\vec{v}_2 = \vec{v}_2 + a \vec{\gamma}_2]$$

$$[\vec{v}_3 = \vec{v}_3 + a \vec{\gamma}_3]$$

$$\vec{v}_n = \vec{v}_{n-1} + a \vec{\gamma}_n$$

average velocity = drift velocity

$$v_d = \frac{\vec{v}_1 + \vec{v}_2 + \dots + \vec{v}_n}{n} = \frac{\vec{v}_1 + \vec{v}_2 + \dots + \vec{v}_n + a(\vec{\gamma}_1 + \dots + \vec{\gamma}_n)}{n}$$

$$\vec{v}_d = \frac{a(\vec{\gamma}_1 + \vec{\gamma}_2 + \dots + \vec{\gamma}_n)}{n}$$

$$\vec{v}_d = \frac{a/\gamma}{n}$$

$\gamma \rightarrow$ average relaxation time

$$\vec{v}_d = \vec{a} \gamma$$

$$\vec{v}_d = -\frac{eE}{m} \gamma$$

$$\vec{v}_d = -\frac{eE \gamma}{m_e}$$

where.


E → Electric field

γ → Relaxation time

m_e → Mass of e⁻

(conductor)

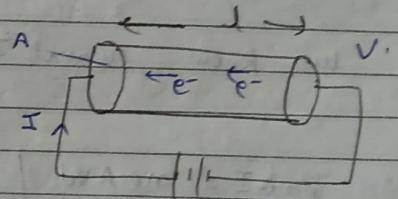* Consider a cylinder of length l which is connected to a external EMF E.



$$\text{Electric field } \vec{E} = \frac{V}{l}$$

Let the e⁻ density = n (electron in per unit volume)

Charge on e⁻ = e

$$\text{No. of e}^- \text{ in } l \text{ length conductor} = n \times (l \times A)$$

$$= n A l$$



$$\text{Total charge} = q = ne$$

$$q = nAld \times e^{-}$$

$$q = e n A l \rightarrow \text{charge on cond.}$$

$d = \frac{\text{distance}}{\text{velocity}}$

$$d = \frac{l}{v_d}$$

$$\text{we know current } I = \frac{q}{t} = \frac{e n A l}{\left(\frac{l}{v_d}\right)}$$

$$I = n e A v_d$$

Current → drift velocity

deduction to Ohm's law.

$$V_d = e E Y$$

(Me) — Mass of e

$$V_d = \frac{e \left(\frac{v}{l}\right) Y}{Me}$$

$$V_d = \frac{e V Y}{Me l}$$

$$I = n e A v_d$$

$$I = n e A \left(\frac{e V Y}{Me} \right)$$

$$I = n e A \left(\frac{e V Y}{Me} \right) = \frac{n e^2 A V Y}{Me}$$

$$\frac{V}{I} = \frac{Me}{n e^2 A Y} \rightarrow \text{constant}$$

by ohms law $R = \frac{Me}{n e^2 A Y}$

Statement

The Lorentz-Drude theory is a classical theory that explains how electrons move in a metal and how this movement contributes to electric current.



Proof of Wiedemann-Franz law.

For metals, the ratio of thermal conductivity to electrical conductivity is directly proportional to the absolute temperature. This ratio is a constant for all metal at a given temperature.

$$\frac{K}{\sigma} \propto T$$

$\frac{K}{\sigma} = LT$, where L is proportionality const. known as Lorentz number.

Derivation

This law is derived from the expression of thermal conductivity (K) and electrical conductivity (σ) of a metal.

We know electrical conductivity of a metal is given by $\sigma = \frac{nc^2Y}{m}$ — (i)

We know that thermal conductivity (K) of a metal is given by,

$$K = \frac{1}{2} nv^2 k Y — (ii)$$

balmer constant

Multiplying (ii) by (i) we get:

$$\frac{K}{\sigma} = \frac{\frac{1}{2} nv^2 k Y}{ne^2 Y/m} = \left(\frac{1}{2} nv^2\right) \frac{K}{e}$$

$$\frac{K}{\sigma} = \left(\frac{1}{2} mv^2\right) \frac{k}{e^2} — (3)$$

The K.E. of free e^- in a metal is given by

$$\frac{1}{2} mv^2 = \frac{3}{2} kT — (4)$$

using 4 in 3

$$\frac{K}{\sigma} = \frac{3}{2} \frac{kT}{e^2} k$$


$$\frac{K}{\sigma} = \left(\frac{3k^2}{2e^2}\right) T$$

$$\boxed{\frac{K}{\sigma} \propto T}$$

$$\boxed{L = \frac{3k^2}{2e^2}}$$

Charging of capacitor through resistance.

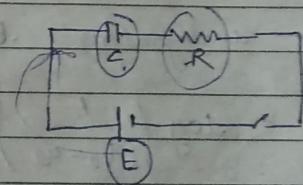The induced emf. of capacitor = $-\frac{dV}{dt}$



Induced E.M.F across capacitor = $\frac{dV}{dt}$

$$\text{P.D. across } R = RI = \boxed{R \frac{dV}{dt}}$$



Equation of R.C circuit for charging becomes.

$$\frac{q_v}{C} + R \frac{dq_v}{dt} = E \quad \text{--- (1)}$$

when ($q_v = q_{v0}$) peak or max charge).

$\frac{dq_v}{dt} = 0$. [at max after that there is no change in charge].

eq(1) becomes

$$E = \frac{q_{v0}}{C}$$

$$\frac{q_v}{C} + R \frac{dq_v}{dt} = \frac{q_{v0}}{C}$$

$$R \frac{dq_v}{dt} = \frac{q_{v0} - q_v}{C}$$

$$\frac{(dq_v)}{q_{v0} - q_v} = \frac{dt}{RC}$$

On integrating both sides.

$$-\log\left(\frac{1}{q_{v0} - q_v}\right) = \frac{t}{RC} + C$$

$$\log(q_{v0} - q_v) = -\frac{t}{RC} + C$$

at $t=0, q_v=0$,

$$\log q_{v0} = C$$

$$\log(q_{v0} - q_v) = -\frac{t}{RC} + (\log q_{v0})$$

$$\log\left(\frac{q_{v0} - q_v}{q_{v0}}\right) = -\frac{t}{RC}$$

$$\log\left(1 - \frac{q_v}{q_{v0}}\right) = -\frac{t}{RC}$$

$$1 - \frac{q_v}{q_{v0}} = e^{-t/RC}$$

$$\frac{q_v}{q_{v0}} = 1 - e^{-t/RC}$$

$$q_v = q_{v0} (1 - e^{-t/RC})$$

* The charging of capacitor is exponential in nature.

* At $t=0$ eq(1) gives $q_v = q_{v0} (1 - e^0)$

$$q_v = 0$$

* At $t=RC \rightarrow$ [time constant for RC circuit]

$$q_v = q_{v0} (1 - e^{-1}) = q_{v0} (1 - \frac{1}{e})$$

$$q_v = q_{v0} (1 - 0.368) = 0.632 q_{v0}$$

$$q_v = 0.632 q_{v0}$$

The time constant of the RC circuit is at the time at which the




the charge on the capacitor become 0.632 times the maximum charge.

* at $t = \infty$

$$q_t = q_0 (1 - e^{-\infty}) = q_0$$

$$\boxed{q_t = q_0}$$

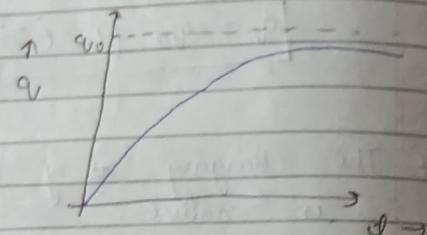Capacitor takes as time for fully charge.



for current.


$$I = \frac{dq}{dt}$$

$$I = \frac{d}{dt} [q_0 (1 - e^{-t/RC})]$$


$$I = -q_0 e^{-t/RC} \cdot -\frac{1}{RC}$$

$$I = +\frac{q_0 e^{-t/RC}}{RC}$$

$$\boxed{I = \frac{q_0}{RC} e^{-t/RC}}$$

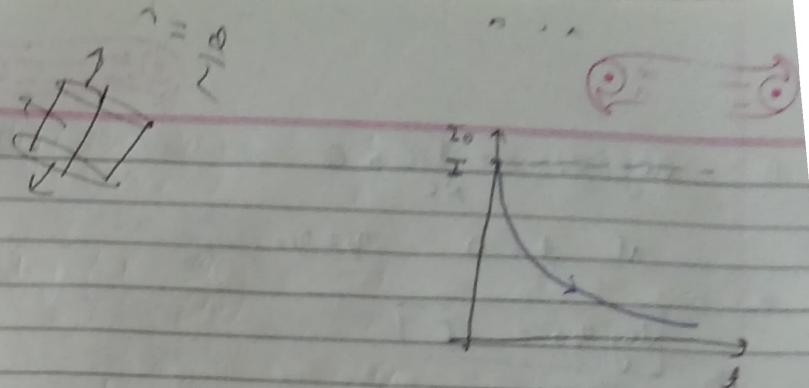

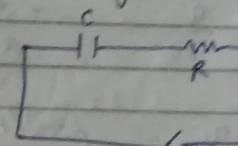Discharging of Capacitor through Resistance.



The induced E.M.F across of C
 $= -\frac{q}{C}$

inducing E.M.F across $C = \frac{q}{C}$

P.D across the $R = \frac{R}{dt}$ [by Ohm's law]

Equation of discharging

$$\frac{q}{C} + R \frac{dq}{dt} = 0 \quad [\text{external E.m.f is removed}]$$

$$R \frac{dq}{dt} = -\frac{q}{C}$$

$$\frac{dq}{q} = -\frac{dt}{RC}$$

integrate $\Rightarrow \int \frac{dq}{q} = \int \frac{dt}{RC}$



$$\log(q) = -\frac{t}{RC} + C$$

$$\text{at } t=0 \quad q=q_0.$$

$$\log q_0 = C$$

$$\rightarrow \log q = \frac{t}{RC} + \log q_0.$$

$$\log \frac{q}{q_0} = -\frac{t}{RC}$$

$$\frac{q}{q_0} = e^{-t/RC}$$

$$q = q_0 e^{-t/RC}$$

$$\# \quad q = q_0 e^{-t/RC} \quad \text{--- (i)}$$

* Exponential in nature

* at $t=0$, $[q=q_0]$.

* at $t=RC$,

$$q = \frac{q_0}{e} = 0.368 q_0$$

$$[q = 0.368 q_0]$$

* at $t=\infty$

$$q = \frac{q_0}{e^\infty} \approx 0.$$

Current variation in discharging.

$$I = \frac{dq}{dt}$$

$$I = \frac{d}{dt} [q_0 e^{-t/RC}] = -q_0 e^{-t/RC} \cdot \frac{1}{RC}$$

$$I = -\frac{q_0}{RC} e^{-t/RC}$$

* At $t=0$ $I = -\frac{q_0}{RC} = I_0$

* At $t=RC$ $I = -0.368 \frac{q_0}{RC} = 0.368 I_0$

* At $t=\infty \Rightarrow I=0$

