

Electro magnetic Induction

The phenomenon in which an emf is induced in a coil due to the change in magnetic flux linked with a coil is called Electromagnetic Induction.

and the direction of induced emf can be obtained by any of the Lenz law or Flemings Right hand Rule.

Faraday's first observations

- whenever there is change in magnetic flux linked with a circuit or a conductor is placed in a varying magnetic field then an E.M.F is induced if the circuit is closed a current is induced which is called induced current.

$$\boxed{\phi \propto i}$$

- The induced emf in a coil is proportional to the rate of change of magnetic flux

$$\epsilon \propto \frac{d\phi_B}{dt}$$

$$\boxed{\epsilon = - \frac{d\phi_B}{dt}}$$

Here the negative sign shows that the induced e.m.f always opposes the change in the magnetic flux.

- If N is the no. of turns in the coil then total induced emf is given by

$$E = -N \frac{d\phi}{dt}$$

- If R is total resistance of the circuit then the induced current is given by

$$i = \frac{E}{R} = -N \frac{d\phi}{R dt}$$

- Integral and differential form of faraday's law.

Change in magnetic flux \rightarrow emf

Acc. to faraday's law

$$E = -\frac{d\phi}{dt} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{s}$$

~~$$also E = \oint \vec{E} \cdot d\vec{l}$$~~

$$\text{Magnetic flux} = \phi_B \quad \int_S \vec{B} \cdot d\vec{s} \quad (i)$$

By the definition of emf the induced e.m.f is equal to the line integral of electric field induced due to varying magnetic field

$$E = \oint_C \vec{E} \cdot d\vec{l} \quad (ii)$$

$$E = -\frac{d\phi_B}{dt} = -\frac{d}{dt} \int_S \vec{B} \cdot d\vec{s}$$

$$\oint_C \vec{E} \cdot d\vec{l} = -\frac{d}{dt} \int_S \vec{B} \cdot d\vec{s}$$

This is the integral form of faraday's law and it shows that the line integral of \vec{E} around the electric circuit is equal to the negative rate of change of magnetic flux passing through the circuit.

By Stokes law

$$\oint \vec{E} \cdot d\vec{l} = \int_S (\nabla \times \vec{E}) \cdot d\vec{s} \quad (iii)$$

$$so \quad \int_S (\nabla \times \vec{E}) \cdot d\vec{s} = -\frac{d}{dt} \int_S \vec{B} \cdot d\vec{s}$$

$$\int_S (\nabla \times \vec{E} + \frac{d\vec{B}}{dt}) \cdot d\vec{s} = 0$$

$$\vec{\nabla} \times \vec{E} + \frac{d\vec{B}}{dt} = 0$$

$$\text{Curl } \vec{E} = - \frac{d\vec{B}}{dt}$$

Since the magnetic field \vec{B} depends on time as well as on position, so instead of $\frac{d\vec{B}}{dt}$, we can write $\frac{\partial \vec{B}}{\partial t}$.

so, $\boxed{\text{Curl } \vec{E} = \vec{\nabla} \times \vec{E} = - \frac{\partial \vec{B}}{\partial t}}$

Self Induction

whenever there is change in a circuit the current in a circuit or coil [change the no. of field lines passing through a circuit or coil] then an e.m.f. is induced in that circuit or coil itself. this phenomenon is called self induction.

Coefficient of self induction

- acc. to Faraday's law the flux linked with the circuit or coil due to the magnetic field is proportional to the current in the coil

$$\phi \propto i$$

$$\phi = Li$$

\hookrightarrow coefficient of self induction / self inductance

if $i = 1$ then $\boxed{\phi = L}$

- * the coefficient of self inductance (L) is equals to the magnetic flux pass through the circuit when 1 ampere current is flows.

$$i = 1 \Rightarrow \phi = L$$

- # acc. to Faraday's second law, the induced emf in the coil is given by

$$\epsilon = - \frac{d\phi}{dt} \quad \text{--- (i)}$$

$$\epsilon = - \frac{d(Li)}{dt} = - L \frac{di}{dt}$$

$$\boxed{\epsilon = - L \frac{di}{dt}}$$

if $\frac{di}{dt} = 1$ then $\boxed{\epsilon = -L}$

- the coefficient of self inductance of a coil is numerically equal to the induced E.m.f. in the coil / circuit when there is unit rate of change of current in the coil.



Say Induction of plain circular coil.

Consider a plain circular coil of radius 'R' having N no. of turns and carrying a current I.

Then we know that the magnetic field at the centre of coil is given by

$$B = \frac{\mu_0 NI}{2R} \quad \text{--- (i)}$$

If we assume that the intensity of \vec{B} is uniform over the entire plane of the coil, then the magnetic flux linked with coil.

$$\phi_B = B \times \text{effective area of the coil}$$

$$\phi_B = B \times (NA)$$

$$A = \pi R^2$$

$$\phi_B = B \times N(\pi R^2)$$

$$\phi_B = \frac{\mu_0 NI}{2R} N \pi R^2$$

$$\phi_B = \frac{\mu_0 N^2 I \pi R}{2} = \frac{\mu_0 \pi N^2 I R}{2}$$

$$\phi = \frac{\mu_0 N^2 \pi R^2 I}{2} = \frac{\mu_0 \pi N^2 I R}{2}$$

$$\text{or } \left[\frac{\phi}{I} = \frac{\mu_0 N^2 R}{2} \right] \quad \text{--- (ii)}$$

$$\text{we know that } L \phi = \phi = L I$$


$$L = \frac{\phi}{I}$$

So, eq (ii) can be written as

$$L = \frac{\mu_0 \pi N^2 R}{2} \quad \rightarrow \text{Say Inductance of plain circular coil}$$

** Say Inductance of a current carrying solenoid

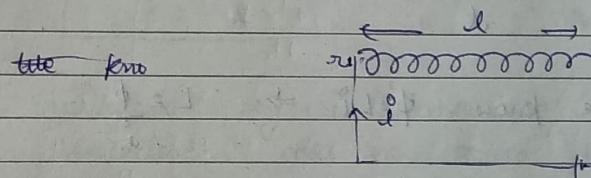Consider a solenoid having radius 'r', length 'l' and have total N no. of turns and carries a current I.



We know that magnetic field on the axis of solenoid

$$B = \frac{\mu_0 N I}{l} = \frac{\mu_0 N i}{l}$$

$i = \text{no. of turns/unit length}$

$$B = \frac{\mu_0 N i}{l} \quad (i)$$

Now we assume that the solenoid is very long. the intensity of magnetic field can be assumed to be uniform inside it at each point.

So, the total magnetic flux linked with the solenoid:

$$\phi = B \times (\text{effective area of solenoid})$$

$$\phi = B \times (N\pi r^2)$$

$$\phi = \frac{\mu_0 N i}{l} (N\pi r^2) \quad \therefore \text{from eq (i)}$$

$$\phi = \frac{\mu_0 N^2 i \pi r^2}{l}$$

$$\frac{\phi}{i} = \frac{\mu_0 N^2 \pi r^2}{l} \quad (iv)$$

$$\because \text{we know } \phi = L i \Rightarrow L = \frac{\phi}{i}$$

eq (ii) can be written as.

$$L = \frac{\mu_0 N^2 \pi r^2}{l}$$

multiply & divide by π

$$L = \frac{\mu_0 N^2 \pi r^2 l}{l^2} \quad \text{in cylindrical form}$$

$$L = \mu_0 n^2 \pi r^2 l = \mu_0 n^2 A l$$

$$L = \mu_0 n^2 A \cdot l$$

where $n = \frac{N}{l}$ & $A = \text{area of solenoid}$
 $A = \pi r^2$

$$L = \frac{\mu_0 N^2}{l} (\pi r^2)$$

let μ_r be the relative permeability of any medium

$$\mu_m = \mu_0 \mu_r$$

permeability
of medium.

$$\text{So } L = \frac{\mu_0 \mu_r N^2}{l} (\pi r^2) \quad \text{Self Inductance of solenoid}$$

* Equivalent self inductance of two inductive coils in series & in parallel

$$xx \quad L = L_1 + L_2 + L_3 + \dots \quad (\text{in series})$$

$$xx \quad \frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots \quad (\text{in parallel})$$



mutual induction :-

If the two coils are placed near each other and the current flowing in one coil is changed then an emf is induced in the other coil. This phenomenon of Electromagnetic Induction is called the mutual induction.

The coil in which current is changed is called primary coil and the other coil kept nearby in which the c.m.f is induced is called secondary coil.

→ Mutual Inductance or Coefficient of Mutual Inductance

- According to Faraday's law, if " i_1 " is the current flowing in the primary coil then the magnetic flux linked with the secondary coil is proportional to the " i_1 ".

$$\therefore \phi_2 \propto i_1$$

$$\boxed{\phi_2 = M i_1}$$

M → Coefficient of Mutual Induction / Mutual Inductance

$$\text{When } i_1 = 1 \Rightarrow \phi_2 = M$$

∴ Therefore the mutual inductance b/w the two coils is numerically equal to the magnetic flux linked with the secondary coil when a unit current flows in the primary coil.

Acc. to Faraday's Second Law :-

If the current flowing in the primary coil is changed, then the induced emf in the secondary coil is

$$E = -\frac{d\phi}{dt}$$


$$E = -\frac{d}{dt} M i_1 = -$$

$$\boxed{E = -M \frac{di_1}{dt}} \quad \text{--- (i)}$$

Mutual Inductance of two circular plain coil

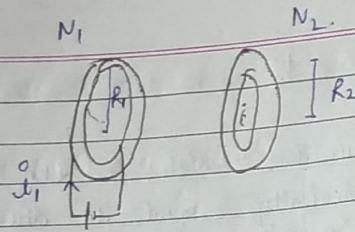Let consider two coils primary & secondary coil, N_1, N_2, R_1 are the no. of turns, R_1 & R_2 are the radius of coil of primary coil and N_2, R_2 is for secondary coil.





Magnetic field due to the primary coil is given by = $\frac{\mu_0 N_1 i_1}{2R_1}$

$$\text{for primary coil } B = \frac{\mu_0 N_1 i_1}{2R_1}$$

$$\rightarrow \text{area of the secondary coil} = N_2 \pi R_2^2$$

flux linked with secondary coil.

$$= B \times \text{area}$$

$$= \phi$$

$$\phi = \frac{\mu_0 N_1 i_1 \times N_2 \pi R_2^2}{2R_1} \quad (i)$$

by the definition of Mutual Inductance

$$\phi_2 \propto i_1$$

$$\phi_2 = M i_1$$

$$M = \frac{\phi_2}{i_1}$$


$$\text{from eq (i)} : \frac{\phi}{i_1} = \frac{\mu_0 N_1 N_2 (\pi R_2^2)}{2R_1}$$

$$\Rightarrow M = \frac{\mu_0 N_1 N_2 (\pi R_2^2)}{2R_1}$$

or Mutual Inductance of two long solenoids

Primary solenoid : N_1, l_1, i_1, r_1

Secondary : N_2, l_2, r_2

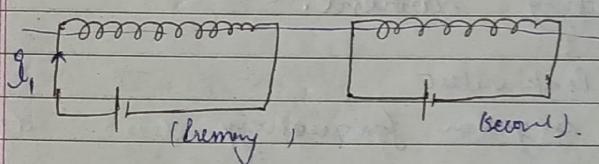

Magnetic field due to primary solenoid

$$B = \mu_0 n_1 i_1 = \mu_0 N_1 i_1 = \frac{\mu_0 N_1 i_1}{l_1}$$

$$\text{area of solenoid (secondary)} = N_2 \pi r_2^2$$

flux linked with sec. solenoid = $B \times \text{area of sol.}$


$$\phi = \frac{\mu_0 N_1 i_1 \times N_2 \pi r_2^2}{l_1}$$

$$\frac{\phi}{i_1} = M = \frac{\mu_0 N_1 N_2 \pi r_2^2}{l_1} = \frac{\mu_0 N_1 N_2 A}{l_1}$$

Mutual Inductance for solenoid

$$M = \frac{\mu_0 N_1 N_2 A}{l_1}$$

Alternating Current is

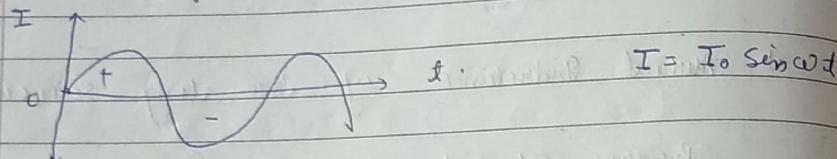

The electric current whose magnitude changes continuously & periodically reverse its direction is called alternating current.

$I_0 \rightarrow$ peak value

$\omega \rightarrow$ angular frequency

$$E = E_0 \sin \omega t$$

↓ ↓
emf max emf


Complex representations of Alternating EMF & Current

$$\boxed{I = I_0 e^{j\omega t}}$$

$$\boxed{E = E_0 e^{j\omega t}}$$

where $j = \sqrt{-1}$

A.C Circuit with pure resistance

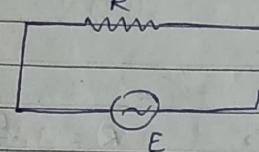

The instantaneous value of alternating e.m.f is given by

$$E = E_0 e^{j\omega t}$$


Acc. to ohm's law

$$\boxed{I = \frac{V}{R}}$$


$$I = \frac{E}{R} = \frac{E_0 e^{j\omega t}}{R} = \left(\frac{E_0}{R}\right) e^{j\omega t}$$

$$\boxed{I = I_0 e^{j\omega t}}$$

graphically

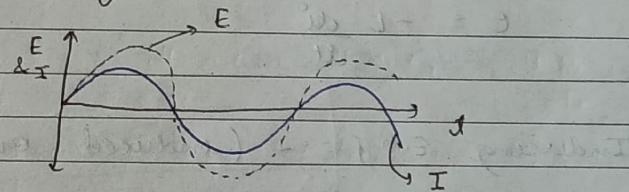

Phaser diagram

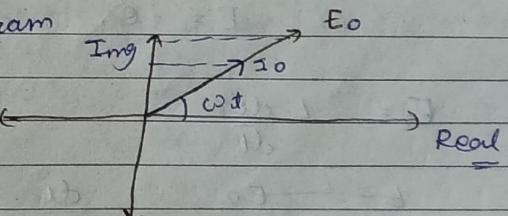

Scanned with OKEN Scanner

Resistance

$$R = \frac{E_0}{I_0}$$


denoted by \mathfrak{J}_2

$$R = \frac{E_0}{\mathfrak{J}^2} = \frac{E_0}{I_0^2} = \frac{E_0}{I_V}$$

$$R = \frac{E_0}{I_V} \rightarrow \text{virtual emf}$$

$$I_V \rightarrow \text{virtual current}$$

A.C circuit with Inductor Only

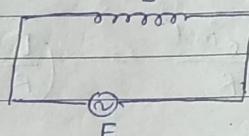

$$E = E_0 e^{j\omega t} \quad \text{--- (i)}$$

to acc. to Faraday's law the
induced emf is given by

$$e = -L \frac{di}{dt}$$

Inducing E.M.F. = - (induced emf)

$$E = -e.$$

$$E_0 = L \frac{di}{dt}$$

$$E = E_0$$

$$\frac{di}{dt} = \frac{E}{L}$$

$$\frac{di}{dt} = \frac{E}{L} = \frac{E_0 e^{j\omega t}}{L}$$

$$di = \frac{E_0 e^{j\omega t}}{L} dt$$

On integrating both sides

$$\int di = i = \frac{E_0}{L} \int e^{j\omega t} dt = \frac{E_0}{j\omega L} e^{j\omega t}$$

$$I = \frac{E_0 e^{j\omega t}}{j\omega L}$$

$$\text{divide & multiply by } j \Rightarrow I = \frac{E_0 j e^{j\omega t}}{j^2 \omega L} = -\frac{E_0 e^{j\omega t}}{\omega L}$$

$$I = -\frac{E_0 j e^{j\omega t}}{\omega L} \quad \text{--- (ii)}$$

$$I = -j \left(\frac{E_0}{\omega L} \right) [\cos \omega t + \sin \omega t] \quad \text{---}$$

$$\therefore e^{-j\pi/2} = \cos \pi/2 - j \sin \pi/2$$

$$e^{-j\pi/2} = -j$$

Put value of $-j$ in eq (ii)

$$I = e^{-j\pi/2} \left(\frac{E_0}{\omega L} \right) e^{j\omega t}$$


$$I = \left(\frac{E_0}{\omega L}\right) e^{j(\omega t - \frac{\pi}{2})}$$

$$I = I_0 e^{j(\omega t - \frac{\pi}{2})} \quad |-(iii) \quad E = E_0 e^{j\omega t}$$


$$I_0 = \frac{E_0}{\omega L} \quad \therefore \omega L = X_L \quad [\text{conductance reactance}]$$

From eq (i) & (ii) the current lags from emf by the phase difference of $\frac{\pi}{2}$.

Graph

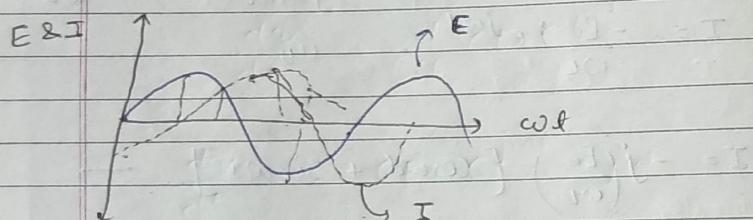

Vector notation

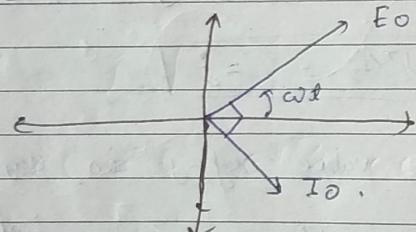

* Reactance due to Inductor.

Inductive Reactance

$$\omega L = \frac{E_0}{I_0} = \frac{\frac{E_0}{\sqrt{2}}}{\frac{I_0}{\sqrt{2}}} = \frac{E_v}{I_v}$$

$$\omega L = \boxed{X_L = \frac{E_v}{I_v}} \quad \begin{array}{l} \text{virtual value of E.M.F} \\ \text{" " " " Current} \end{array}$$

$$\text{As } X_L = \omega L$$


$$\boxed{X_L = 2\pi f V_L}$$

$$X_L \propto v \text{ (frequency)}$$

for DC $v=0$

$$\boxed{X_L = 0}$$

A.C circuit with capacitor only.

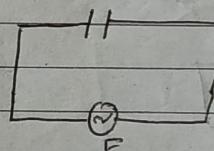

$$E = E_0 e^{j\omega t} \quad |-(i)$$



induced emf is given by

$$e = -\frac{v}{c}$$

$E = -e \rightarrow$ by lenz law.

$$E = \frac{v}{c}$$

$$v = CE$$

$$v = CE_0 e^{j\omega t}$$

we know that current $I = \frac{dv}{dt}$

$$\frac{dv}{dt} = \frac{d}{dt} CE_0 e^{j\omega t}$$

$$\frac{dv}{dt} = CE_0 e^{j\omega t} \cdot j\omega$$

$$\frac{dv}{dt} = j\omega C E_0 e^{j\omega t}$$

$$e^{j\pi/2} = j$$




$$\frac{dv}{dt} = I = e^{j\pi/2} \cdot C E_0 e^{j\omega t}$$

$$i = \frac{E_0}{(j\omega C)} e^{j(\omega t + \pi/2)}$$

$$I_0 = \frac{E_0}{j\omega C}$$

$$i = i_0 e^{j(\omega t + \pi/2)} \quad (ii)$$

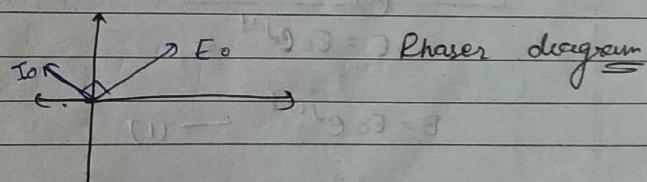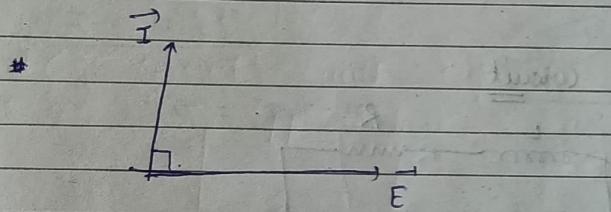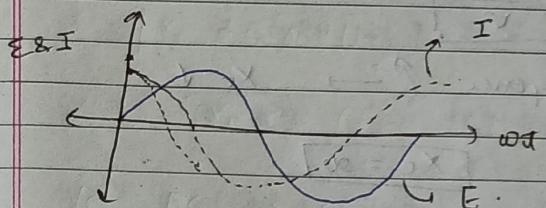from eq (i) & (ii) the alternating current leads the EMF by the phase angle of $\pi/2$.



Resistance due to Capacitor
Capacitive reactance

$$\frac{1}{\omega C} = X_C = \frac{E_0}{I_0} = \frac{E_v}{I_v}$$

$$X_C = \frac{1}{\omega C} = \frac{E_v}{I_v}$$


$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi v C}$$

$$X_C \propto \frac{1}{v}$$

as frequency $\uparrow \rightarrow X_C \downarrow$.

for DC - $X_C = \infty$

L-R circuit

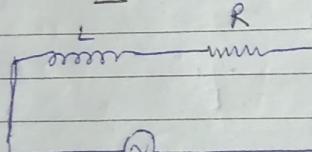

$$E = E_0 e^{j\omega t}$$

$$E = E_0 e^{j\omega t} \quad \text{--- (i)}$$

Potential diff. across R = $I_0 R$

P.D across Inductor = $I_0 j\omega L$

$e^{j\pi/2}$ Current lags behind in inductor by $\pi/2$.

The peak value is given by

$$E_0 = I_0 R + I_0 j\omega L$$

$$E_0 = I_0 [R + j\omega L]$$

$$E_0 = I_0 Z$$


where $Z \rightarrow$ impedance (complex) of L-R circuit
 $Z = [R + j\omega L]$

$$|Z| = \sqrt{R^2 + \omega^2 L^2} = \sqrt{R^2 + X_L^2}$$

$$Z = |Z| (\cos \phi + j \sin \phi) = |Z| e^{j\phi}$$

$$Z = |Z| e^{j\phi}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

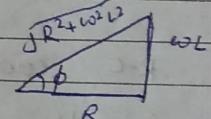


Instantaneous value of current is given by

$$I = \frac{E}{Z} = \frac{E_0 e^{j\omega t}}{|Z| e^{j\phi}}$$

$$I = \frac{E_0}{|Z|} e^{j(\omega t - \phi)} \quad \text{--- (ii)}$$



(n)

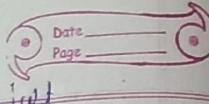



$$I = I_0 e^{j(\omega t - \phi)}$$

$$E = E_0 e^{j\omega t}$$


Current in L-R circuit lags behind the E.M.F. by the phase difference of ϕ :

$$I_0 = \frac{E_0}{|Z|} = \frac{E_0}{\sqrt{R^2 + X_L^2}}$$

graph

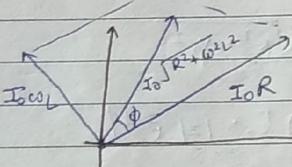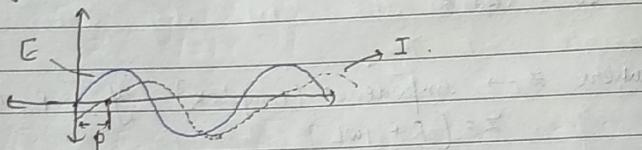

R-C circuit

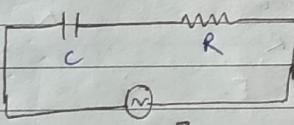

$$E = E_0 \sin \omega t$$

$$E = E_0 e^{j\omega t}$$

Peak value of alternating E.M.F. across R
 $V_R = I_0 R$

$$\text{the emf across } C = \frac{I_0}{j\omega C}$$

$$V_C = -j \frac{I_0}{\omega C}$$

$\frac{1}{j}$ → current leads in capacitive circuit $\frac{1}{\omega C}$

$$E_0 \sin \omega t = I_0 \left(\frac{-j}{\omega C} + \frac{R}{E_0} \right)$$

$$E_0 = I_0 \left[R - \frac{j}{\omega C} \right]$$

$$E_0 = I_0 Z$$

$$Z = R - \frac{j}{\omega C} = \text{impedance of R-C circuit}$$

$$|Z| = \sqrt{R^2 + \frac{1}{(\omega C)^2}} = \sqrt{R^2 + X_C^2}$$

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$Z = |Z| e^{j\phi} = |Z| [\cos \phi + j \sin \phi]$$

$$Z = \sqrt{R^2 + X_C^2} e^{j\phi}$$

$$\text{if current is given by } I = \frac{E}{Z} = \frac{E_0 e^{j\omega t}}{Z}$$



To potential drop across capacitor and Resistor

$$V_T = E = VR + VC$$

$$E = IR - \frac{jI}{wC}$$

$$\frac{E}{I} = R - j\frac{1}{wC} = Z$$

Z can be written as

$$Z = |Z| \cos \phi = j |Z| \sin \phi = |Z| e^{-j\phi}$$


$$Z = |Z| e^{-j\phi}$$

$$I = \frac{E}{Z} = \frac{E_0 e^{j\omega t}}{|Z| e^{-j\phi}}$$

$$I = I_0 e^{j(\omega t + \phi)}$$

$$I_0 = \frac{E_0}{\sqrt{R^2 + X_L^2}}$$

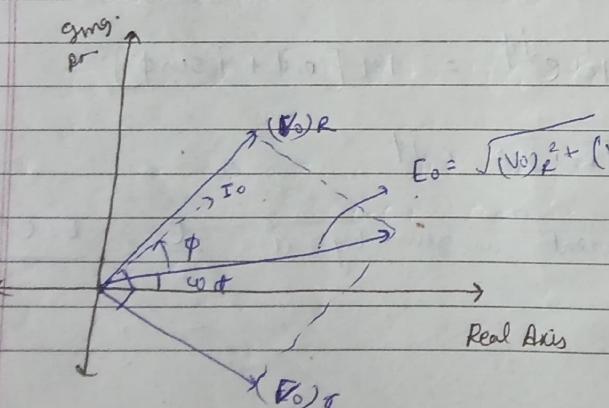
Current leads potential by the phase difference of ϕ .



Series L-C-R

Let a source of alternately emf given by

$$E = E_0 e^{j\omega t}$$

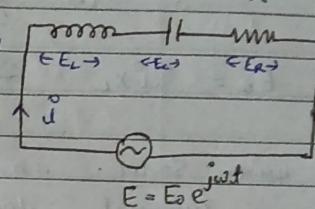

be connected to a series combination of a resistor, inductor, capacitor

$$E = E_0 e^{j\omega t}$$

Let 'I' be the current drawn in the circuit at time 't'

• Voltage drop across capacitor C at time 't' is given by

$$E_C = I \times \text{Resistance by capacitor} = I \times X_C$$

$$E_C = I j X_C \quad \text{--- (i)}$$

In capacitor the ~~Emf~~ Emf lags behind current by the phase diff. of $\pi/2$ so we multiply $-j$ on R.H.S in eq. (i).

$$E_C = -j I X_C \quad \text{--- eq (ii)}$$

• Voltage drop across resistor in the circuit at time 't'.

$$E_R = I R$$

$$E_R = j R \quad \text{--- eq (iii)}$$



voltage drop across inductor L at time t is given by

$$E_L = \dot{i} X_L \quad (\text{iv})$$

Since in inductive circuit the current lags behind by the EMF with a phase diff. of $\frac{\pi}{2}$ so we multiply by j on R.H.S of eq (iv)

$$E_L = j \dot{i} X_L \rightarrow (\text{v})$$

Total voltage drop in the circuit

$$E = E_L + E_C + E_R$$

∴ add eq (ii), (iii), (iv)

~~$E = E_0 e^{j\omega t}$~~ $E = \dot{i} [R + jX_L - jX_C]$

$$E = \dot{i} [R + j(X_L - X_C)]$$

$$\frac{E}{\dot{i}} = Z = R + j(X_L - X_C)$$

where Z is the impedance of the L-C-R circuit.

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

also we can write

$$Z = |Z| [\cos \phi + j \sin \phi]$$

$$= Z = \sqrt{R^2 + (X_L - X_C)^2} e^{j\phi}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} e^{j\phi}$$

we know that $E = \dot{i} Z$

$$\text{from this } \dot{i} = \frac{E}{Z} = \frac{E_0 e^{j\omega t}}{\sqrt{R^2 + (X_L - X_C)^2} e^{j\phi}}$$

$$\frac{E}{Z} = \frac{E_0}{\sqrt{R^2 + (X_L - X_C)^2}} \cdot e^{j(\omega t - \phi)}$$

$$\therefore \dot{i} = I_0 e^{j(\omega t - \phi)}$$

$$I = I_0 e^{j(\omega t - \phi)}$$


$$\text{here } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

If $X_L > X_C$, the current lags behind by emf with phase diff. of ϕ .

If $X_C > X_L$ then current leads by emf by the phase of ϕ .




(iv) If $X_L > X_C$

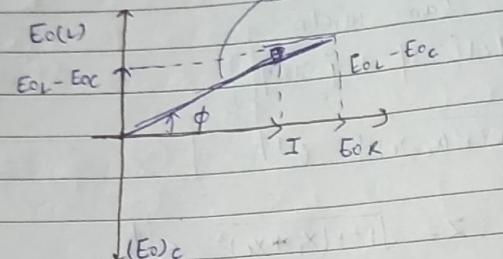

$$E_0 = \sqrt{E_{0R}^2 + (E_0 - E_0c)^2}$$

Case V if $X_C > X_L$.

$$\frac{1}{\omega C} > \omega L$$

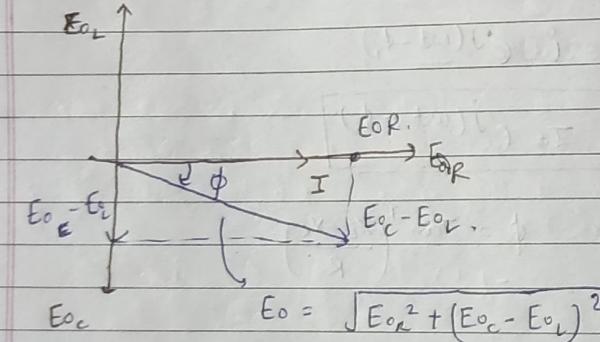

$$E_0 = \sqrt{E_{0R}^2 + (E_0c - E_0L)^2}$$


Case VI when $X_L = X_C$

$$\omega L = \frac{1}{\omega C}$$


$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = 0$$

Current & E_m are in same phase.
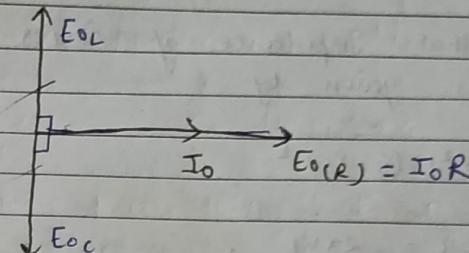
$$\Theta = \phi = \frac{E_0}{R} \text{ max current}$$



Parallel L-C-R circuit

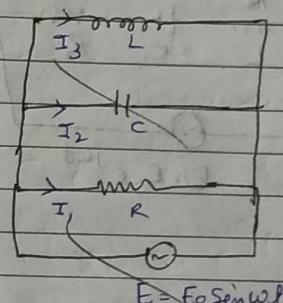

$$I_1 = \frac{E_0}{R} \sin(\omega t) \quad (i)$$

$$I_2 = \frac{E_0}{X_C} \sin(\omega t + \pi/2) \quad (ii)$$

$$I_3 = \frac{E_0}{X_L} \sin(\omega t - \pi/2) \quad (iii)$$

$$V_C = V_L = V_R$$

at


* Series Resonant Circuit

we know that Impedance of series LCR circuit is given by.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

where $X_L = \omega L = 2\pi f L$,
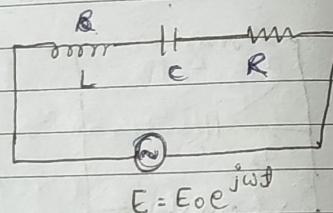
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$



) at Resonance.

$$X_L = X_C$$


$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

↳ Resonant frequency

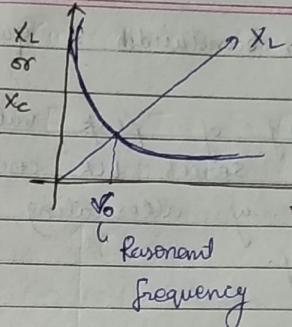


The value of resonant frequency of the circuit depends only on the value of Inductance (L) & capacitance (C).

If $V = V_0$, we have $Z = R = \text{minimum}$

for the frequency f_0 , the impedance of the circuit is minimum and the corresponding current is maximum. The variation of alternating current with frequency f is shown in fig.

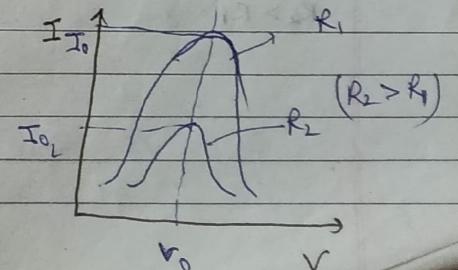In series resonant circuit, the current flowing in the circuit is max. hence it is called acceptor circuit. Such circuits are used in tuning of radio & t.v.



Q) Sharpness of resonance, bandwidth & quality factor

when an alternating emf of peak value E_0 is applied to a series LCR circuit, then the peak value of alternating current in it is given by.

$$I_0 = \frac{E_0}{Z} = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

where Z is the impedance of LCR circuit.


at resonance,

$$\omega L = \frac{1}{\omega C}, Z = R \text{ (minimum)}$$

$$I_0 = \frac{E_0}{R} \text{ (max)} \quad \& \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

The variation of I_0 with ' ω ' is shown in fig for 2 diff values of R

$$R_2 > R_1$$

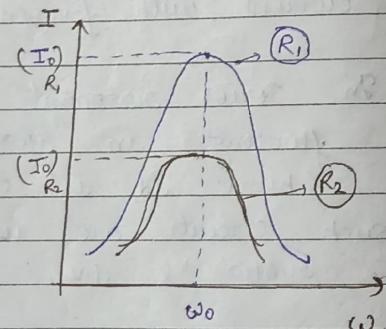

$$\frac{I_0}{\sqrt{2}} = 0.707 I_0 \rightarrow \text{Rms current } I = I_0$$

for each curve, there are 2 frequencies ω_1 and ω_2

(Called lower and upper cut off frequencies) such that current falls to $\frac{1}{\sqrt{2}}$ times the max current I_0

then the difference $\omega_2 - \omega_1$ is called bandwidth ($\Delta\omega$) of Series L.C.R circuit

$$\Delta\omega = \omega_2 - \omega_1$$

Sharpness of Resonance = $\frac{\text{Resonant frequency}}{\text{Bandwidth}}$

$$= \frac{\omega_0}{\omega_2 - \omega_1} \quad (\Delta\omega)$$

$$\text{from graph} = \omega_2 = \omega_0 + \frac{\Delta\omega}{2}$$

$$\& \omega_1 = \omega_0 - \frac{\Delta\omega}{2}$$

$$Q) I_0 = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \dots(i)$$

$$\text{at } \omega = \omega_2 \text{ we have } I_a = \frac{I_0}{\sqrt{2}}$$



so from eqn (1) we get:

$$(I_0)_m = \frac{E_0}{\sqrt{R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2}}$$

$$I_{0m} = \frac{E_0}{R}$$

$$\frac{E_0}{R\sqrt{2}} = \frac{E_0}{\sqrt{R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2}}$$

$$R\sqrt{2} = \sqrt{R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2}$$

Square both sides

$$2R^2 = R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2$$

$$R^2 = \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2$$

$$R = \omega_0 L - \frac{1}{\omega_0 C}$$

$$\therefore \text{we know } \omega_0 = \omega_0 + \frac{\Delta\omega}{2}$$

$$R = \left(\omega_0 + \frac{\Delta\omega}{2}\right)L - \frac{1}{\left(\omega_0 + \frac{\Delta\omega}{2}\right)C}$$

$$R = \omega_0 \left[1 + \frac{\Delta\omega}{2\omega_0} \right]L - \frac{1}{\omega_0 C \left[1 + \frac{\Delta\omega}{2\omega_0} \right]}$$

$$R = \omega_0 L \left(1 + \frac{\Delta\omega}{2\omega_0} \right) - \frac{1}{\omega_0 C \left(1 + \frac{\Delta\omega}{2\omega_0} \right)}$$

at Resonance ω_0

$$\left[\omega_0 L = \frac{1}{\omega_0 C} \right]$$

$$R = \omega_0 L \left(1 + \frac{\Delta\omega}{2\omega_0} - \frac{1}{1 + \frac{\Delta\omega}{2\omega_0}} \right)$$

$$R = \omega_0 L \left[\left(1 + \frac{\Delta\omega}{2\omega_0} \right) - \left(1 + \frac{\Delta\omega}{2\omega_0} \right)^{-1} \right]$$

$$\left[(1+x)^{-n} = 1-nx \right], \text{ highest power are neglected}$$

$$R = \omega_0 L \left[\left(1 + \frac{\Delta\omega}{2\omega_0} \right) - 1 + \frac{\Delta\omega}{2\omega_0} \right]$$

$$R = \omega_0 L \left(\frac{2\Delta\omega}{2\omega_0} \right)$$

$$R = L \Delta\omega$$

$$\boxed{\Delta\omega = \frac{R}{L}}$$

$$\Delta\omega = \frac{R}{L}$$

$$\text{Sharpness of resonance} = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\frac{R}{L}} = \frac{\omega_0 L}{R}$$

$$\text{Sharpness of resonance} = \frac{\omega_0 L}{R}$$



Quality factor (Q) of series LCR circuit is given by

$$Q = \frac{\omega_0 L}{R} = \frac{\omega_0}{\frac{R}{L}} = \frac{\omega_0}{\Delta\omega}$$

$$Q = \frac{\omega_0}{\Delta\omega}$$

Parallel Resonant Circuit

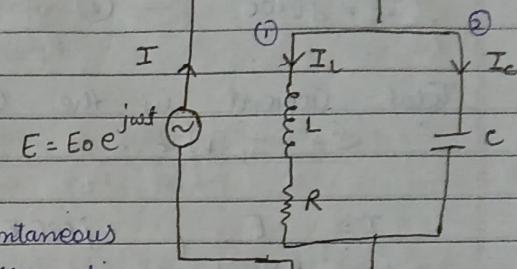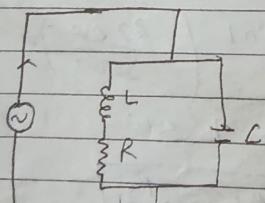A parallel resonant circuit consists of a series combination of inductor and resistor connected in parallel to a capacitor. This parallel combination is then connected to a source of alternating emf.



Let the instantaneous value of alternating emf at time t is given by

$$E = E_0 e^{j\omega t}$$

Voltage drop across branch ①

$$V_L + V_R$$

$$= I_L j\omega L + I_R R$$

$$E = I_L (j\omega L + R) \quad [\text{voltage leads current by } \pi/2 \text{ so multiply by } j]$$

$$E = I_L (j\omega L + R)$$

$$E = I_L (j\omega L + R)$$

$$I_L = \frac{E}{j\omega L + R} \rightarrow (i)$$

Voltage drop across branch ② -

$$= V_C$$

$$E = I_C X_C - j = -\frac{I_C j}{\omega L}$$

$$I_C = \frac{E \omega L}{-j} = j E \omega L$$

$$I_C = jE\omega C \quad \text{--- (1)}$$

Total current in the circuit is given by
 $I = I_L + I_C$

$$I = \frac{E}{R+j\omega L} + j\omega C E$$

$$I = E \left[\frac{1}{R+j\omega L} + j\omega C \right]$$

$$\frac{I}{E} = \frac{1}{R+j\omega L} + j\omega C = \frac{1}{Z}$$

The reciprocal of impedance (Z) of a circuit is known as admittance (Y).

$$Y = \frac{1}{Z} = \frac{1}{\frac{E}{I}} = \frac{I}{E}$$

$$Y = \frac{1}{R+j\omega L} + j\omega C$$

$$\frac{1}{Z} = \frac{1}{R+j\omega L} + j\omega C$$

$$Y = \frac{1}{Z} = \frac{R-j\omega L}{R^2+\omega^2 L^2} + j\omega C$$

$$Y = \frac{1}{Z} = \frac{R-j\omega L}{R^2+\omega^2 L^2} + j\omega C$$

$$Y = \frac{1}{Z} = \frac{R-j\omega L + j\omega C (R^2+\omega^2 L^2)}{R^2+\omega^2 L^2}$$

$$Y = \frac{1}{Z} = \frac{R-j\omega L + j\omega C R^2 + j\omega^3 C L^2}{R^2+\omega^2 L^2}$$

$$Y = \frac{1}{Z} = \frac{R - j(\omega L - \omega C R^2 - \omega^3 C L^2)}{R^2+\omega^2 L^2}$$

From above equation it is clear that for a given values of $L, C & R$ the admittance (Y) will be maximum or the impedance maximum if

$$\omega L - \omega C R^2 - \omega^3 C L^2 = 0$$

$$\omega(L - CR^2 - \omega^2 CL^2) = 0$$

$$L - CR^2 - \omega^2 CL^2 = 0$$

$$L - CR^2 = \omega^2 CL^2$$

$$\frac{L}{CL^2} - \frac{CR^2}{CL^2} = \omega^2$$



$$\frac{1}{CL} - \frac{R^2}{L^2} = \omega^2$$

$$\omega = \sqrt{\frac{1}{CL} - \frac{R^2}{L^2}}$$


$$2\pi v_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$v_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

→ Resistor Circuit.

v_0 is called "Resonant Frequency" In parallel resonant circuit at frequency equals to resonant frequency (v_0) the (Z) of the circuit is max, so current in it will be minimum
So parallel resonant circuits are called "Resistor circuits"

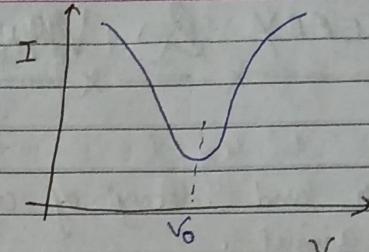These circuits are used as "filter circuits" in radios to block the currents of undesired frequency.



Power in Alternating current

$$\text{Power } P = V i \quad (\text{in current electricity})$$

So, here in AC both V & i varies with time power will also vary with time

$$P(t) = V(t) i(t)$$

$$\text{let } V = V_0 \sin \omega t \quad I = I_0 \sin(\omega t + \phi)$$

$$P(t) = V_0 \sin \omega t \cdot I_0 \sin(\omega t + \phi)$$